

# Verilog Notes - 161 Lab

Jose M. Rodriguez  
jrodr050@ucr.edu  
Chung 464

Embedded System Lab  
UC Riverside

May 1, 2017

# FMS Mealy Vs Moore

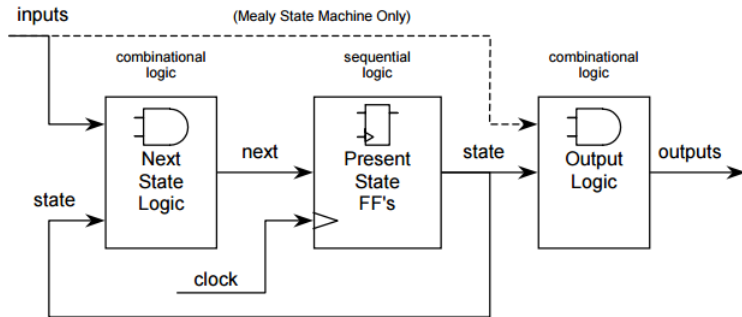


Figure 1 - FSM Block Diagram

Source : "Coding And Scripting Techniques For FSM Designs With Synthesis-Optimized, Glitch-Free Outputs." by Cummings, C.E.

# FMS State Diagram

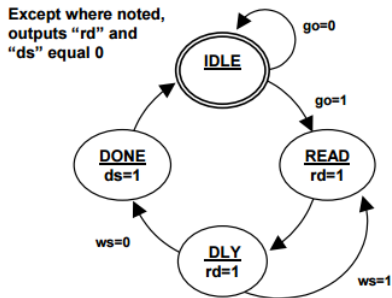


Figure 2 - FSM1 State Diagram

# FMS Coding - Right Code

```
module fsm1a (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input  go, ws;
    input  clk, rst_n;

    parameter [1:0] IDLE = 2'b00,
                  READ  = 2'b01,
                  DLY   = 2'b10,
                  DONE  = 2'b11;

    reg [1:0] state, next;

    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else        state <= next;

    always @(state or go or ws) begin
        next = 2'bx;
        case (state)
            IDLE: if (go) next = READ;
                  else   next = IDLE;

            READ:      next = DLY;

            DLY:  if (ws) next = READ;
                  else   next = DONE;

            DONE:      next = IDLE;

        endcase
    end

    assign rd = (state==READ || state==DLY);
    assign ds = (state==DONE);
endmodule
```

State register,  
sequential  
always block

Next state,  
combinational  
always block

Continuous  
assignment  
outputs

# FMS Coding - Right Code

```
module fsm1 (ds, rd, go, ws, clk, rst_n);
    output ds, rd;
    input  go, ws;
    input  clk, rst_n;
    reg    ds, rd;

    parameter [1:0] IDLE = 2'b00,
                  READ  = 2'b01,
                  DLY   = 2'b10,
                  DONE  = 2'b11;

    reg [1:0] state, next;

    always @(posedge clk or negedge rst_n)
        if (!rst_n) state <= IDLE;
        else       state <= next;

    always @(state or go or ws) begin
        next = 2'bx;
        ds = 1'b0;
        rd = 1'b0;
        case (state)
            IDLE: if (go)    next = READ;
                  else      next = IDLE;

            READ: begin      rd = 1'b1;
                           next = DLY;
                      end

            DLY:  begin      rd = 1'b1;
                           if (ws) next = READ;
                           else   next = DONE;
                      end

            DONE: begin      ds = 1'b1;
                           next = IDLE;
                      end

        endcase
    end
endmodule
```

State register,  
sequential  
always block

Next state & outputs,  
combinational always  
block

# Multi-Stage Coding (Pipelines )

 


Figure 4 - Multi-stage module partition with registered outputs

# Multi-Stage Coding (Pipelines )

Example : Compute in hardware the following function using a multi-stage design ( Taylor Expansion )

$$\sqrt{1+x} \approx 1 + \frac{x}{2} - \frac{x^2}{8} + \frac{x^3}{16} - \frac{5x^5}{128} + \frac{7x^5}{256} \text{ for } |x| < 1$$

Proposed solution :

- Compute each factor in one stage .
- Register the output of each stage.
- Add the results as the computation progress.
- Reuse the previous computations i.e. reuse  $x^{n-1}$  to compute  $x^n$ .

# Multi-Stage Coding (Pipelines )

First, we design and implement one stage.

 


Figure 4 - Multi-stage module partition with registered outputs



# Multi-Stage Coding (Pipelines )

- Inputs
- Clock
- Enable
- Add flag
- $X$
- $X^{n-1}$
- Multiplication and Division Factor
- Running Result
- Parameters

- Outputs
- Valid
- New result
- $X^n$

# Multi-Stage Coding (Pipelines )

First, we design and implement one stage.

```
4
5 module fixpbinomialstep #( parameter NBITS = 16, parameter Q = 8 )
6 (
7   input wire clk,
8   input wire enable,
9   input wire add ,
10  input wire [NBITS-1:0] xn,
11  input wire [NBITS-1:0] xnacum ,
12  input wire [NBITS-1:0] mfactor ,
13  input wire [NBITS-1:0] dfactor ,
14  input wire [NBITS-1:0] oresult ,
15  output reg valid ,
16  output reg [NBITS-1:0] xnacumn ,
17  output reg [NBITS-1:0] result
18 ) ;
19
20 wire [NBITS-1 :0] t1, t2, t3 ;
21
22 fixpmult #( .NBITS (NBITS), .Q(Q) ) m1 ( .a( xn ), .b( xnacum ), .r(t1) ) ;
23 fixpmult #( .NBITS (NBITS), .Q(Q) ) m2 ( .a(mfactor), .b(t1), .r(t2) ) ;
24
25 assign t3 = (add == 'b1) ? $signed(oresult) + $signed(t2 >>> dfactor) :
26                      $signed(oresult) - $signed(t2 >>> dfactor) ;
27
28 always @( posedge clk ) begin
29
30     valid    <= enable ;
31     xnacumn  <= t1 ;
32     result   <= t3 ;
33
34 end
35 endmodule
36
```

# Multi-Stage Coding (Pipelines )

Now, all stages together

 


Figure 4 - Multi-stage module partition with registered outputs

# Multi-Stage Coding (Pipelines)

Next, all stages together


```
35 // -----
36 // First Iteration r = 1 + x/2
37 // -----
38 wire [NBITS-1:0] ONE;
39 assign ONE = { {NBITS-Q-1{1'b0}}, {1'b1}, {Q{1'b0}} };
40
41 assign r0 = $signed(ONE) + $signed(x0 >> 1);
42
43
44 // -----
45 // Second Iteration 2 Cycle rn = r - (1/8) x ^ 2
46 // -----
47
48 fixpbinomialstepaux #( .NBITS (NBITS), .Q(Q) )
49 c1 (
50   .clk(clk), |
51   .enable(iter0),
52   .add(1'b0),
53   .xn(x0),
54   .xnacum(xn0),
55   .dfactor(32'd3),
56   .oresult(r0),
57   .valid(iter1),
58   .xnacumn(xnacum1),
59   .result(r1) );
60
```

```
61 // -----
62 // Third Iteration 3 Cycle rn = r + (1/16) x ^ 3
63 // -----
64
65 fixpbinomialstepaux #( .NBITS (NBITS), .Q(Q) )
66 c2 (
67   .clk(clk),
68   .enable(iter1),
69   .add(1'b1),
70   .xn(x1),
71   .xnacum(xnacum1),
72   .dfactor(32'd4),
73   .oresult(r1),
74   .valid(iter2),
75   .xnacumn(xnacum2),
76   .result(r2) );
77
78 // -----
79 // Four Iteration 3 Cycle rn = r - (1/128) x ^ 4
80 // -----
81
82 wire [NBITS-1:0] FIVE;
83 assign FIVE = { {NBITS-Q-3{1'b0}}, {3'b101}, {Q{1'b0}} };
84
85 fixpbinomialstep #( .NBITS (NBITS), .Q(Q) )
86 c3 (
87   .clk(clk),
88   .enable(iter2),
89   .add(1'b0),
90   .xn(x2), |
91   .xnacum(xnacum2),
92   .mfactor(FIVE),
93   .dfactor(32'd7),
94   .oresult(r2),
95   .valid(iter3),
96   .xnacumn(xnacum3),
97   .result(r3) );
98
```

- Good coding styles for FSM.
- FSMs implemented in two or three blocks ( One sequential the others combinatorial )
- Introduced the idea of digital pipelines.
- Pipelines are make of combinatorial and sequential components.
- The divide and conquer approach at work.

# Questions ...

# Lab Notes

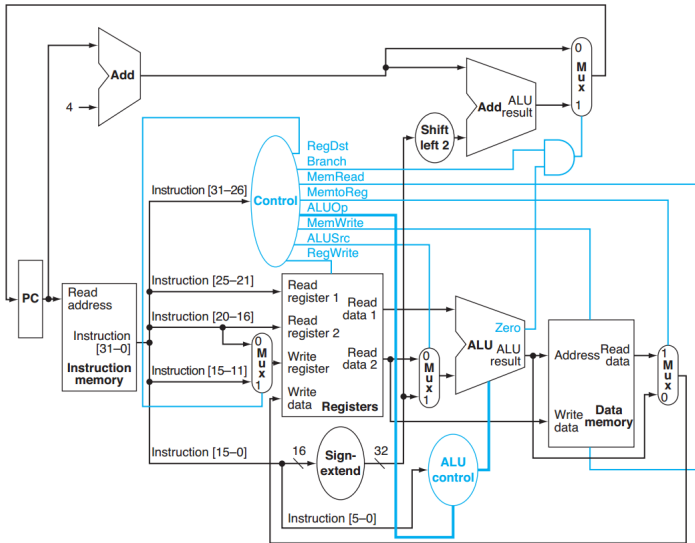

**FIGURE 4.17 The simple datapath with the control unit.** The input to the control unit is the 6-bit opcode field from the instruction.